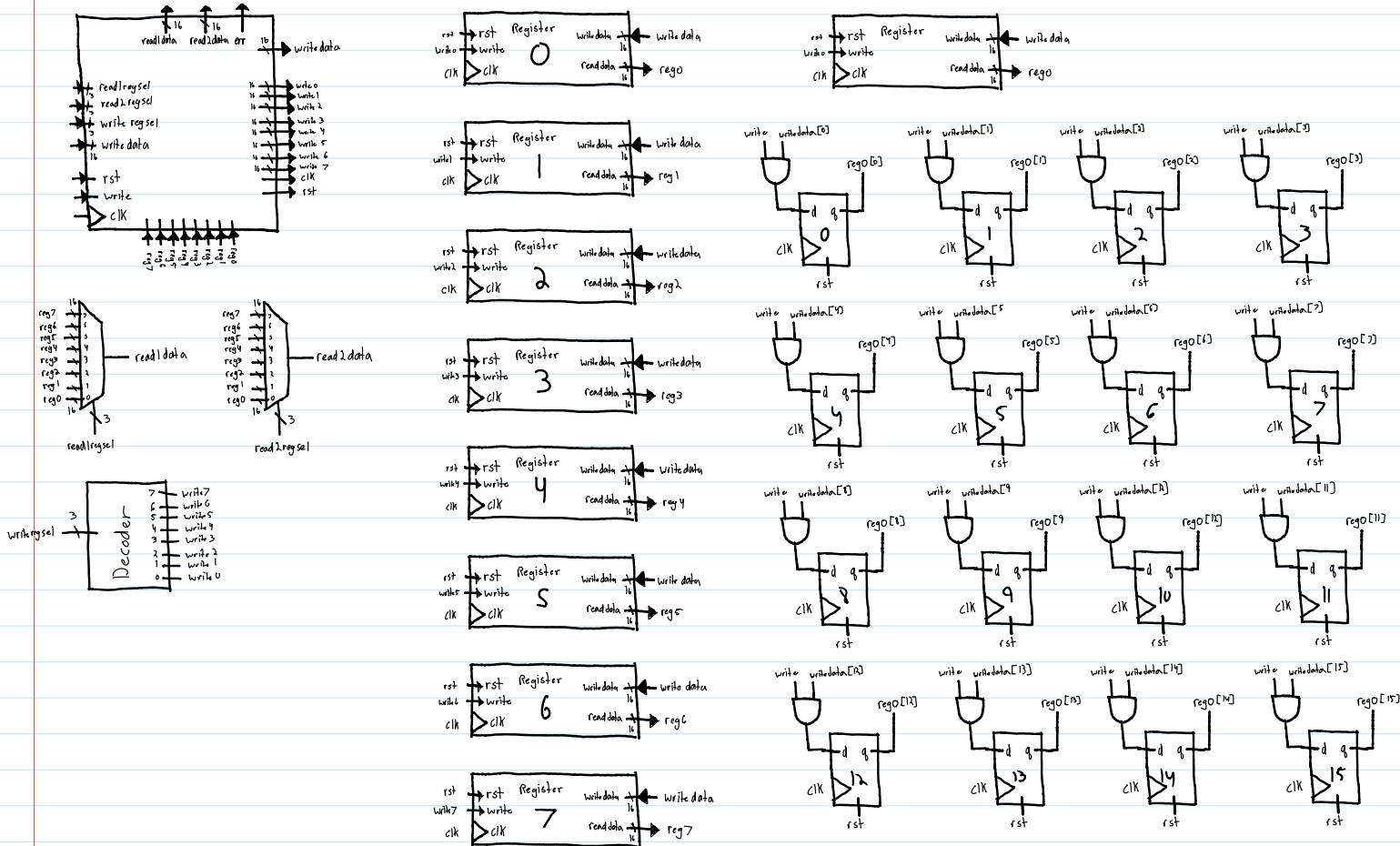


Homework 3

Thursday, February 18, 2016 3:29 PM

Problem 1

Inputs: clk
 rst
 $write$
 $read1regsel [2:0]$
 $read2regsel [2:0]$
 $write reg sel [2:0]$
 $writedata [15:0]$



Problem 2

Inputs: $clock$
 rst_rst

