
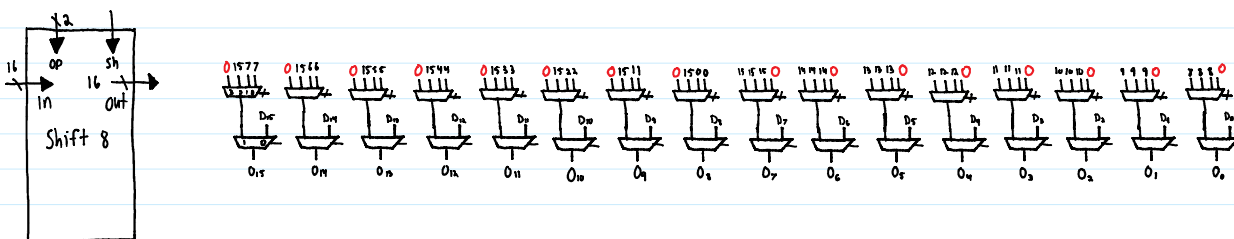
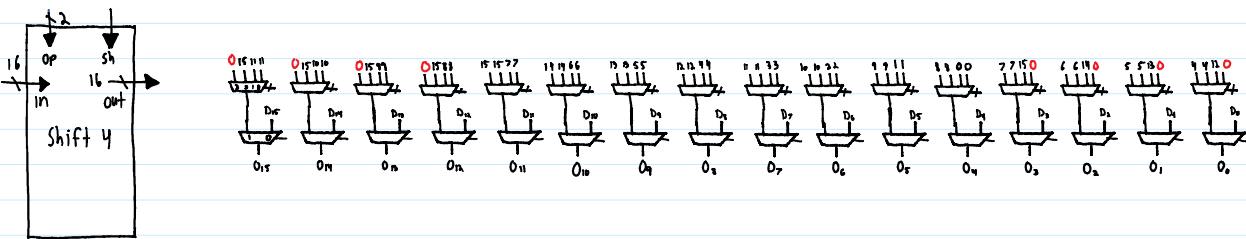
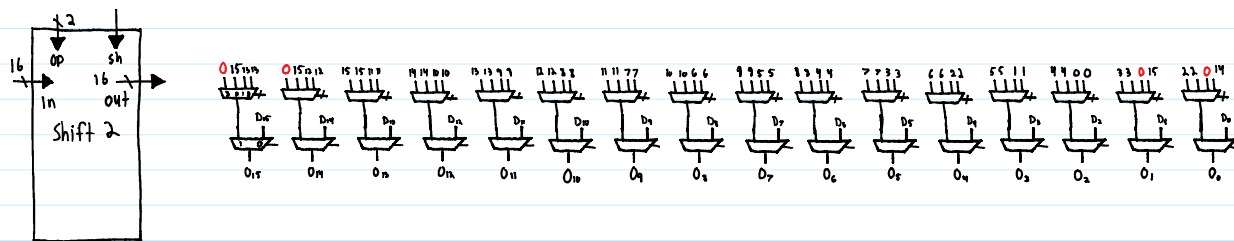
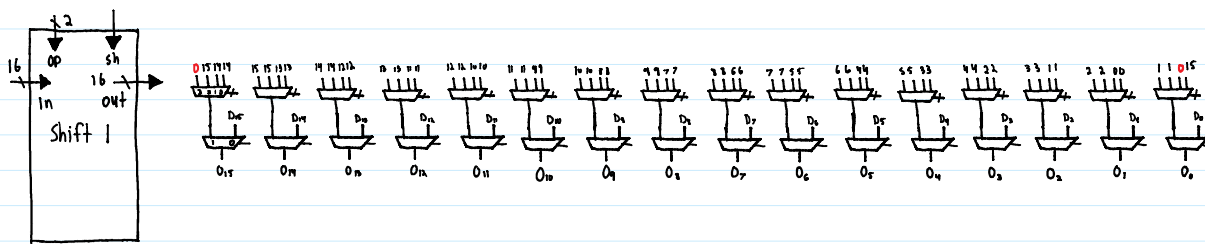


## Homework 2



Sunday, February 7, 2016 2:16 PM
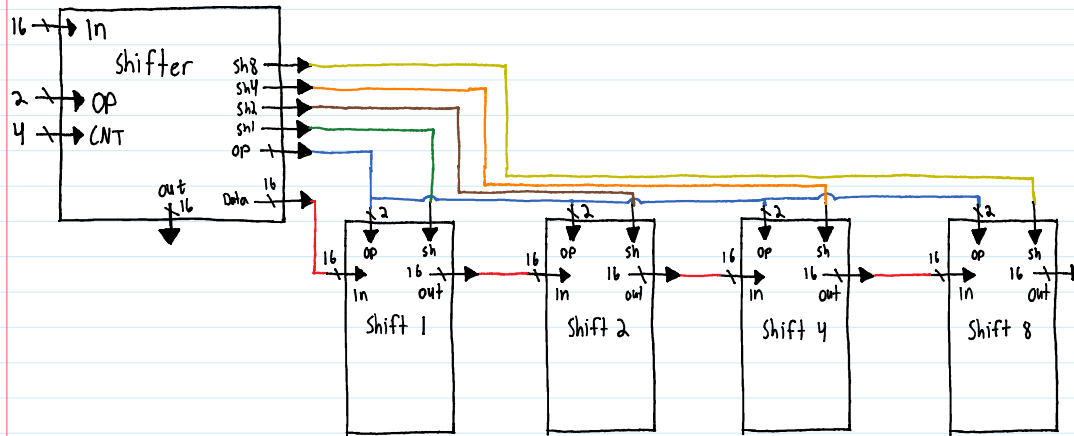
### Problem 1 (Barrel Shifter)

- 00 Rotate Left
- 01 Shift Left
- 10 Shift Right arithmetic
- 11 Shift Right logical



### Problem 2 (ALU)

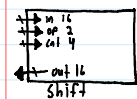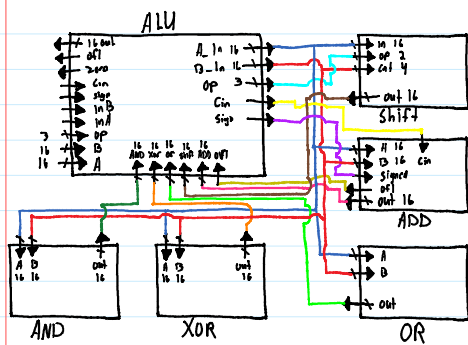

See Problem #1

